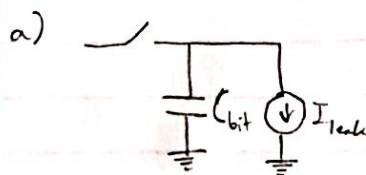


Homework #8

#2 DRAM



$$C_{bit} = 18 \text{ fF} (1 \text{ fF} = 10^{-15} \text{ F})$$

$$V_{init} = 1.2 \text{ V} \text{ (must be } \geq 0.8 \text{ V to retain value of 1)}$$

$$V_{min} = 0.8 \text{ V}$$

$$Q = CV$$

$$Q_{bit} = C_{bit} V_{bit}$$

← differentiate

$$I_{leak} = \frac{dQ_{bit}}{dt} = C_{bit} \frac{dV_{bit}}{dt}$$

$$I_{leak} = \frac{0.4 \text{ V}}{0.001 \text{ s}} (18 \times 10^{-15} \text{ F})$$

$$= 7.2 \text{ pA}$$

$$b) C = \epsilon \frac{A}{d}$$

$$= \epsilon \frac{1024 \times (0.5 \times 10^{-6} \text{ m}) (0.5 \times 10^{-6} \text{ m})}{0.1 \times 10^{-6} \text{ m}}$$

$$= 22.65 \times 10^{-15} \text{ F}$$

$$c) Q_{bit} = C_{bit} V_{bit} \text{ (initially)}$$

$$C_{bit} V_{bit} = (C_{bit} + C_{wire}) V_{column} \text{ (final)}$$

$$\frac{18}{38} V_{bit} = V_{column}$$

$$\text{So } \Rightarrow \begin{cases} 0.568 \text{ V if initial is 1.2 V} \\ 0 \text{ V if initial is 0 V} \end{cases}$$

d) Rearranging formula from c)

$$V_{column} = \frac{C_{bit} V_{bit}}{C_{bit} + C_{wire}}$$

$$0.4 \text{ V} = \frac{(18 \text{ fF})(1.2 \text{ V})}{18 \text{ fF} + C_{max}}$$

$$C_{max} = 36 \text{ fF}$$


Using part b)

$$36 \times 10^{-15} \text{ F} = \epsilon \frac{x (0.5 \times 10^{-6} \text{ m})^2}{0.1 \times 10^{-6} \text{ m}}$$

$$x = 1626$$

#3 Mag-lev Train

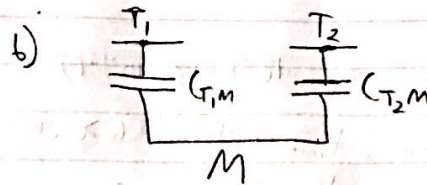
a)
$$C_{T1M} = C_{T2M} = \epsilon \frac{WL_{\text{Train}}}{h}$$



c) We want C_{eff} . They're in series $\rightarrow \frac{1}{C_{\text{eff}}} = \frac{1}{C_{T1M}} + \frac{1}{C_{T2M}}$

$$C_{\text{eff}} = \frac{\epsilon WL_{\text{Train}}}{2h}$$

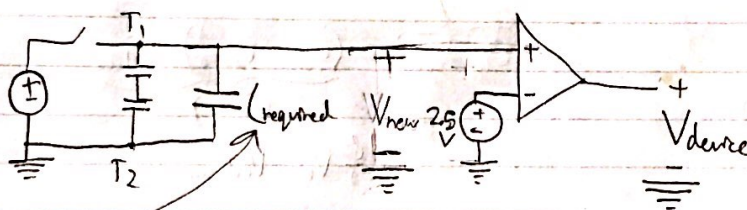
d) C_{eff} is inversely related to distance between train & track.



$$C_{\text{required}} = 8.85 \times \frac{100 \cdot 0.01}{200^{-2}} = 442.5 \text{ pF}$$


V_{new} measures the voltage.

e) Break the strips up into blocks.

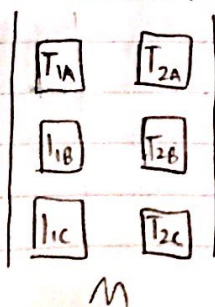

#4) It's Finally Raining

a)

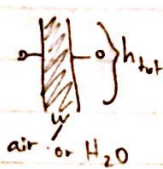

$$C_{\text{empty}} = \frac{\epsilon_{\text{air}} h_{\text{tot}} w}{w} = \boxed{\epsilon h_{\text{tot}}}$$

$$C_{\text{full}} = \frac{\epsilon_{\text{H2O}} h_{\text{tot}} w}{w} = \boxed{81 \epsilon h_{\text{tot}}}$$

b) $C_{\text{H2O}} = \frac{\epsilon_{\text{H2O}} h_{\text{H2O}} w}{w} = 81 \epsilon h_{\text{H2O}}$ $C_{\text{air}} = \frac{\epsilon_{\text{air}} (h_{\text{tot}} - h_{\text{H2O}}) w}{w} = \epsilon (h_{\text{tot}} - h_{\text{H2O}})$

Since the 2 capacitors are ||, we just add them.

$$\boxed{C_{\text{tank}} = \epsilon (h_{\text{tot}} + 80 h_{\text{H2O}})}$$

c)

ϕ_1 $Q_{C_{\text{tank}}} = Q_{C_{\text{known}}} = C_{\text{eff}} V_{\text{in}} = \left(\frac{C_{\text{tank}} C_{\text{known}}}{C_{\text{tank}} + C_{\text{known}}} \right) V_{\text{in}}$


ϕ_2 charge share

$$2(\checkmark) = V_{\text{out}} (C_{\text{tank}} + C_{\text{known}})$$

in ϕ_2 , they are 'in parallel'

$$\boxed{V_{\text{out}} = 2 V_{\text{in}} \left(\frac{C_{\text{tank}} C_{\text{known}}}{(C_{\text{tank}} + C_{\text{known}})^2} \right)}$$

d)

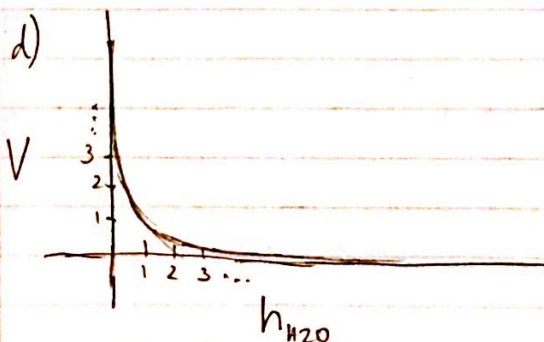

f) $[V_o] = V \checkmark$ $[h_{\text{H2O}}] = m \checkmark$

e) $\left(\frac{1}{C_{\text{tank}}} + \frac{1}{C_{\text{known}}} \right) (C_{\text{tank}} + C_{\text{known}}) = \frac{2 V_{\text{source}}}{V_o}$

$$\frac{C_{\text{tank}}}{C_{\text{known}}} + \frac{C_{\text{known}}}{C_{\text{tank}}} = 2 \left(\frac{V_{\text{in}}}{V_o} - 1 \right)$$

quadratic formula w/ $\frac{C_{\text{tank}}}{C_{\text{known}}} = x$

$$h_{\text{water}} = \frac{h_{\text{tot}}}{80} \left(\frac{V_{\text{source}}}{V_o} - 2 + \sqrt{\left(\frac{V_{\text{source}}}{V_o} - 1 \right)^2 - 1} \right)$$

#5)

Skanda Suresh #3031861340

Mohan Ganesan #24199173

Adhyyan Narang #26433045

We worked together on the entire homework.