

**This homework is due March 1, 2016, at Noon.**

**Optional Problems:** We **do not** grade these problems. Nevertheless, you are responsible for learning the subject matter within their scope.

**Bonus Problems:** We **do** grade these problems. Doing them will provide an unspecified amount of extra credit; not doing them will not affect your homework grade negatively. We will specify if the problem is in or out of scope.

**1. Homework process and study group**

Who else did you work with on this homework? List names and student ID's. (In case of hw party, you can also just describe the group.) How did you work on this homework?

Working in groups of 3-5 will earn credit for your participation grade.


**Solution:** I worked on this homework with...

I first worked by myself for 2 hours, but got stuck on Problem 5 so I went to office hours on...

Then I went to homework party for a few hours, where I finished the homework.


**2. Mechanical Circuits**

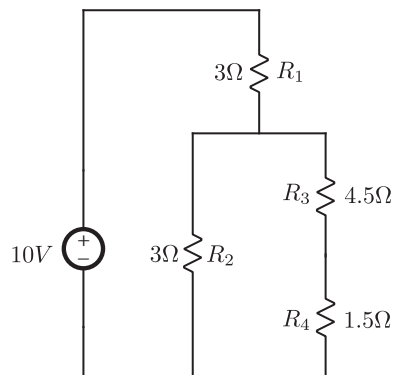- (a) Find the voltages across and currents flowing through all the resistors.



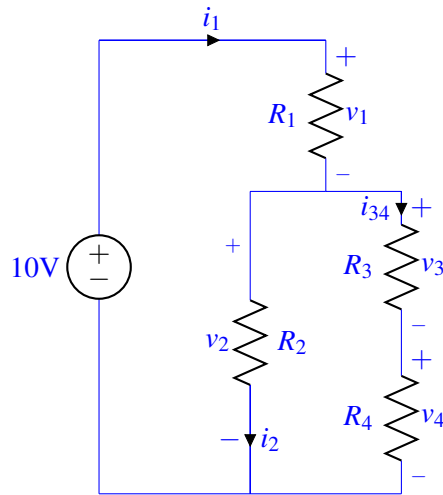**Solution: Approach 1 – KCL / KVL:**

First, label all the 'junctions' or 'nodes':



Now set up your KCL / KVL equations:

$$i_1 = i_2 + i_{34} \quad (1)$$

$$v_1 = i_1 \cdot R_1 \quad (2)$$

$$v_2 = i_2 \cdot R_2 \quad (3)$$

$$v_3 = i_{34} \cdot R_3 \quad (4)$$

$$v_4 = i_{34} \cdot R_4 \quad (5)$$

$$v_2 = v_3 + v_4 = i_{34} \cdot (R_3 + R_4) \quad (6)$$

$$10 = v_1 + v_2 = v_1 + v_3 + v_4 \quad (7)$$

You can solve as a system of equations:

$$\frac{10 - v_2}{R_1} = \frac{v_2}{R_2} + \frac{v_2}{R_3 + R_4}$$

$$\frac{10}{R_1} = v_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3 + R_4} \right)$$

$$\frac{10}{3} = v_2 \left( \frac{1}{3} + \frac{1}{3} + \frac{1}{4.5 + 1.5} \right) = v_2 \cdot \frac{5}{6} \Rightarrow v_2 = 4$$

$$v_1 = 10 - v_2 = 6 \text{ V} \quad i_{34} = \frac{4}{4.5 + 1.5} = \frac{2}{3} \text{ A} \quad v_3 = i_{34} R_3 = 3 \text{ V} \quad v_4 = i_{34} R_4 = 1 \text{ V}$$

Alternatively, you could set it up as a matrix and use ipython / numpy to solve.

$$\begin{bmatrix} 1 & -1 & -1 & 0 & 0 & 0 & 0 \\ -3 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & -3 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & -4.5 & 0 & 0 & 1 & 0 \\ 0 & 0 & -1.5 & 0 & 0 & 0 & 1 \\ 0 & 0 & -6 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_{34} \\ v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 10 \end{bmatrix}$$

This returns the array:

$$\begin{bmatrix} i_1 \\ i_2 \\ i_{34} \\ v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 2 \\ \frac{4}{3} \\ \frac{2}{3} \\ 6 \\ 4 \\ 3 \\ 1 \end{bmatrix}$$

**Approach 2 –** We will first calculate the effective resistance seen from the voltage source to find the current supplied by the voltage source. The resistances  $R_3$  and  $R_4$  are in series hence have effective resistance of  $6\Omega$ . They are connected in parallel to a  $R_2$  resistance yielding an effective resistance of

$$\left(\frac{1}{6} + \frac{1}{3}\right)^{-1} = 2\Omega.$$

This resulting effective resistance is in series to  $R_1$ , yielding an effective resistance of  $5\Omega$ . Hence the current supplied by the voltage source is

$$10V/5\Omega = 2A.$$

Let us denote the voltage drop across  $R_i$  as  $V_i$ , and the current flowing through  $R_i$  and  $I_i$ . We have  $I_1 = 2A$  current flowing through  $R_1$ , hence we have  $V_1 = 6V$ . The remaining voltage  $10V - 6V = 4V$  is across both  $R_2$  and the sequence of resistors  $R_3$  and  $R_4$ . Hence,  $I_2 = 4V/3\Omega = 4/3A$ . Furthermore,  $I_3 = 4V/6\Omega = 2/3A$ . Combining all, we get the following voltages and currents,

$$I_1 = 2A,$$

$$I_2 = \frac{4}{3}A,$$

$$I_3 = I_4 = \frac{2}{3}A,$$


$$V_1 = 6V,$$

$$V_2 = 4V,$$

$$V_3 = 3V,$$


$$V_4 = 1V.$$

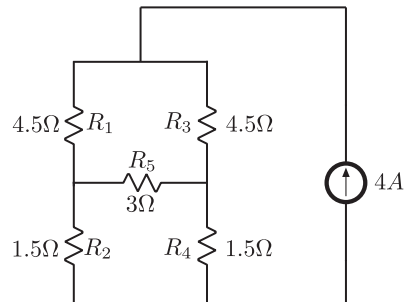- (b) Find the voltages across and currents flowing through all the resistors.



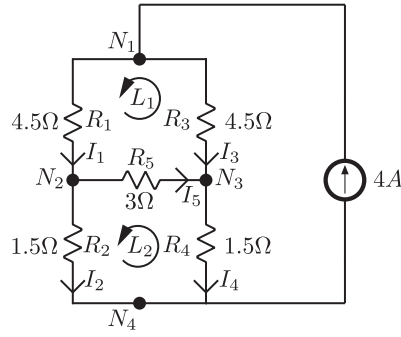**Solution:**

**Approach 1 –** Let us denote the voltage drop across  $R_i$  as  $V_i$ , and the current flowing through  $R_i$  and  $I_i$ ; and let us label the nodes with  $N_1, N_2, N_3$  and  $N_4$  as shown in the figure below.



At the nodes we have the following KCL equalities

$$I_1 + I_3 = 4A, \quad (\text{at node } N_1)$$

$$I_5 = I_1 - I_2, \quad (\text{at node } N_2)$$

$$I_5 = I_4 - I_3, \quad (\text{at node } N_3)$$

$$I_2 + I_4 = 4A. \quad (\text{at node } N_4)$$

Furthermore, we can write the KVL around the loops  $L_1$  and  $L_2$

$$4.5I_3 - 4.5I_1 - 3I_5 = 0, \quad (8)$$

$$1.5I_4 + 3I_5 - 1.5I_2 = 0. \quad (9)$$

$$(10)$$

Multiplying equation (9) by three and subtracting equation (8) we get

$$\begin{aligned} 0 &= 3(1.5I_4 + 3I_5 - 1.5I_2) - (4.5I_3 - 4.5I_1 - 3I_5) \\ &= 4.5(I_4 - I_3 + I_4 - I_3) + 12I_5. \end{aligned}$$

Substituting the equations coming from KCL at nodes  $N_2$  and  $N_3$  we get

$$\begin{aligned} 0 &= 4.5(I_4 - I_3 + I_4 - I_3) + 12I_5 \\ &= 4.5(I_5 + I_5) + 12I_5 \\ &= 21I_5, \end{aligned}$$

which shows that the current through resistor  $R_5$  needs to be

$$I_5 = 0.$$

Substituting this in equation (9) and (8) we get

$$I_2 = I_4, \quad (11)$$

$$I_1 = I_3, \quad (12)$$

and the KCL at nodes  $N_2$  and  $N_3$  then say that

$$I_1 = I_2$$

$$I_3 = I_4,$$

hence we have

$$I_1 = I_2 = I_3 = I_4.$$

By the KCL at node  $N_1$  we have

$$I_1 + I_3 = 4A$$

which says

$$I_1 = I_2 = I_3 = I_4 = 2A.$$


Using the currents we have found, we can calculate

$$V_1 = V_3 = 4.5\Omega \times 2A = 9V,$$

$$V_2 = V_4 = 1.5\Omega \times 2A = 3V,$$

$$V_5 = 3\Omega \times 0A = 0V.$$

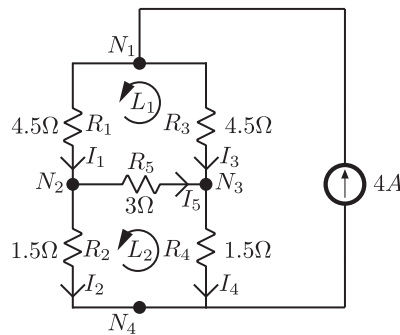**Approach 2** – We can also use nodal analysis, and write our system in terms of unknown voltages (instead of unknown currents, as in the previous approach). Let node  $N_4$  be our reference ground, at voltage  $0V$ . Then the three unknown nodal voltages are at nodes  $N_1, N_2, N_3$ . Let these nodal voltages be  $u_1, u_2, u_3$  respectively. The figure is reproduced below for convenience:



Then write the KCL constraints (current conservation) at each node:

$$+(u_2 - u_1)/R_1 + (u_3 - u_1)/R_3 + 4 = 0 \quad \text{(Current conservation at } N_1)$$

$$+(u_1 - u_2)/R_1 + (u_3 - u_2)/R_5 + (0 - u_2)/R_2 = 0 \quad \text{(Current conservation at } N_2)$$

$$+(u_1 - u_3)/R_1 + (u_2 - u_3)/R_5 + (0 - u_3)/R_2 = 0 \quad \text{(Current conservation at } N_3)$$

Substituting the actual values of the resistors and solving this system, we find:  $u_1 = 12V, u_2 = 3V, u_3 = 3V$ . Then all the branch currents can be found from these nodal voltages, using Ohm's Law.

**Approach 3** – It was possible to notice “by symmetry” that there is no current across the middle resistor  $R_5$ , and further that the currents across the two remaining branches must be equal. It is a good intuition that symmetry of a circuit will result in symmetry in its electric flow. This is in fact generally true, but requires a more careful argument to justify.<sup>1</sup> See the “Uniqueness and Symmetry” problem on Discussion 7A for details on how to invoke symmetry arguments, and when they apply.

<sup>1</sup>One might argue that “nature has no preference”, and hence cannot break symmetries. However, this is not necessarily true – there are many situations where small random fluctuations can break initial symmetries. For example, in unstable equilibria (like balancing a pen on end).

### 3. Cell Phone Battery

As great as smartphones are, one of the main gripes about them is that they need to be recharged too often. Suppose a Samsung Galaxy S3 requires about 0.4 W to maintain a signal as well as its regular activities (dominated by the display and backlight in many cases). The battery provides 2200 mAh at a voltage of 3.8V until it is completely discharged.

- (a) How long will one full charge last you?

**Solution:** 400 mW of power at 3.8V is about 105.26mA of current. A battery that can provide 1mAh can provide 1mA for an hour, so our 2200mAh battery can source 105.26mA for  $2200/105.26 = 20.9$  hours, almost a full day.

An alternative approach is to say 2200 mAh at 3.8V is  $2200 \times 3.8 = 8360$  milliwatt-hours. 0.4 W is 400 mW, so  $8360/400 = 20.9$  hours is how long the charge will last.

- (b) Suppose the cell phone battery is completely discharged and you want to recharge it completely. How much energy (in J) is this? How much charge (in C) must be pumped through the battery?

**Solution:** The battery is rated for 2200 mAh at 3.8V, which gives  $2200 \times 3.8 = 8360$  milliwatt-hours. A joule is equivalent to watt-second, and there are 3600 seconds in an hour, so our battery has  $8360 \times 3600 = 30,096,000$  mJ, or 30,096 J. A milliamp is 0.001 coulombs per second, so a milliamp-hour is  $0.001 \times 3600 = 3.6$  coulombs. Then a 2200 mAh battery needs  $3.6 \times 2200 = 7,920$  coulombs of charge to be moved to be fully recharged. An electron has charge approximately  $1.602 \times 10^{-19}$  C, so 7,920 coulombs is  $7920/1.602 \times 10^{-19} \approx 4.94 \times 10^{22}$  electrons.

- (c) Suppose PG&E charges \$0.16 per kWh. Every day, you completely discharge the battery and recharge it at night. How much will recharging cost you for the month of October (31 days)?

**Solution:** 2200 mAh at 3.8V is  $2200 \times 3.8 = 8,360$  milliwatt-hours, or 0.00836 kWh. At \$0.16 per kWh, that is  $0.16 \times 0.00836$  dollars per day, or  $0.16 \times 0.00836 \times 31 = 0.0414656$ , or about 4 cents a month.

- (d) You are fed up with PG&E, gas companies, and Duracell/Energizer/etc. You want to generate your own energy and decide to buy a small solar cell (e.g. [http://ixdev.ixys.com/DataSheet/XOB17-Solar-Bit-Datasheet\\_Mar-2008.pdf](http://ixdev.ixys.com/DataSheet/XOB17-Solar-Bit-Datasheet_Mar-2008.pdf)) for \$1.50 on digikey. It delivers 40 mA at 0.5 V in bright sunlight. Unfortunately, now you have can only charge your phone when the sun is up. Using one solar cell, do you think there is enough time to charge a completely discharged phone every day? How many cells would you need to charge a completely discharged battery in an hour? How much will it cost you per joule if you have one solar cell that works for 10 years (assuming you can charge for 16 hours a day)? Do you think this is a good option?

**Solution:** One solar cell provides 40 mA at 0.5 V in bright sunlight, which is  $40 \times 0.5 = 20$  mW. Note that this is considerably less than the phone's power consumption of 400 mW, so we should expect the solar panel to take much longer to charge than the  $\approx 1$  day of battery life. In fact,  $2200 \times 3.8 \times (20)^{-1} = 418$  hours to charge using one panel, so even if the sun was bright all day, it would not be enough to charge the phone. It would take 418 panels to charge the battery in an hour. The total amount of energy collected over 10 years, assuming 16 hours of operation per day, is approximately (neglecting leap-years, etc.)  $10 \times 365 \times 16 \times 40 \times 0.5 = 1,168,000$  mWh, or 1.168 kWh. That is  $1.50/1.168 \approx 1.28$  dollars per kWh, or  $1.50 \times (1.168 \times 3600 \times 1000) = 3.57 \times 10^{-7}$  dollars per joule. This particular solar panel doesn't provide enough power to charge the phone's battery during the daylight hours (with a reasonable number of panels). However, if the panel lasts long enough, the cost per joule is actually pretty reasonable.

- (e) The battery has a lot of internal circuitry that prevents it from getting overcharged (and possibly exploding!) as well as transferring power into the chemical reactions used to store energy. We will model

this internal circuitry as being one resistor with resistance  $R_{\text{bat}}$ , which you can set to any non-negative value you want. Furthermore, we'll assume that all the energy dissipated across  $R_{\text{bat}}$  goes to recharging the battery. Suppose the wall plug and wire can be modeled as a 5V voltage source and 200 m $\Omega$  resistor, as pictured in Fig. ?? . What is the power dissipated across  $R_{\text{bat}}$  for  $R_{\text{bat}} = 1\text{m}\Omega$ , 1 $\Omega$ , and 10k $\Omega$ ? How long will the battery take to charge for each of those values of  $R_{\text{bat}}$ ?

**Solution:** The energy stored in the battery is 2200mAh at 3.8V, which is  $2.2 \times 3.8 = 8.36\text{Wh}$ . We can find time to charge by dividing this energy by power in W to get time in hours.

For  $R_{\text{bat}} = 1\text{m}\Omega$ , the total resistance seen by the battery is  $1\text{m}\Omega + 200\text{m}\Omega = 201\text{m}\Omega$  (because the wire and  $R_{\text{bat}}$  are in series), so by Ohm's law, the current is  $5/0.201 = 24.88\text{A}$ . The voltage drop across  $R_{\text{bat}}$  is (again by Ohm's law)  $24.88 \times 0.001 = 0.025\text{V}$ . Then power is  $0.025 \times 24.88 = 0.622\text{W}$  and the total time to charge the battery is  $8.36/0.622 = 13.44$  hours.

Similarly, for 1 $\Omega$ , the total resistance seen by the battery is  $1 + .200 = 1.2\Omega$ , the current through the battery is  $5/1.2 = 4.17\text{A}$ , and the voltage across the battery is by Ohm's law  $4.17 \times 1 = 4.17\text{V}$ . Then the power is  $4.17 \times 4.17 = 17.39\text{W}$  and the total time to charge the battery is  $8.36/17.39 = 0.48$  hours, about 29 minutes. (Thanks to Kailas Vodrahalli for spotting the mistake in the original solutions.)

For 10k $\Omega$ , the total resistance seen by the battery is  $10000 + .200 = 10000.2\Omega$ , the current through the battery is  $5/10000.2 \approx 0.5\text{mA}$ , and the voltage across the battery is by Ohm's law  $0.5\text{mA} \times 10\text{k}\Omega \approx 5\text{V}$  (up to 2 significant figures). Then the power is  $5\text{V} \times 0.5\text{mA} = 2.5\text{mW}$  and the total time to charge the battery is  $8.36/0.0025 = 3,344$  hours.

- (f) (Bonus) Suppose you forgot to charge your phone overnight, and you're in a hurry to charge it before you leave home for the day. What should we set  $R_{\text{bat}}$  to be if we want to charge our battery as quickly as possible? How much current will this draw? How long will it take to charge?

*Hint: what choice of  $R_{\text{bat}}$  maximizes the power dissipated across the resistor?*

**Solution:** To minimize the time it takes to charge the battery, we want to minimize the time it takes to accumulate the amount of energy to fill the battery. For constant power (which we have because the circuit is not time varying),  $E = PT$ , so to minimize time  $T$  we should maximize power  $P$ .

We know  $P = I_R^2 R_{\text{bat}}$ , so we want to find  $R_{\text{bat}}$  that maximizes that expression. First observe that the 200m $\Omega$  resistor and  $R_{\text{bat}}$  are in series, so we can treat them together as one equivalent resistor with resistance  $200\text{m}\Omega + R_{\text{bat}}$ . Then by Ohm's law  $I_R = \frac{5\text{V}}{200\text{m}\Omega + R_{\text{bat}}}$ . We then maximize

$$P = \left( \frac{5}{0.2 + R_{\text{bat}}} \right)^2 \times R_{\text{bat}}$$

where  $R_{\text{bat}}$  is in Ohms and  $P$  is in Watts.

The  $R_{\text{bat}}$  that maximizes  $P$  is  $R_{\text{bat}} = 200\text{m}\Omega$ . To show this, find the derivative of  $P$  with respect to  $R_{\text{bat}}$  and set it equal to zero.

$$\frac{dP}{dR_{\text{bat}}} = 25 \left( \frac{1}{(0.2 + R_{\text{bat}})^2} + \frac{-2R_{\text{bat}}}{(0.2 + R_{\text{bat}})^3} \right) = 25 \frac{0.2 - R_{\text{bat}}}{(0.2 + R_{\text{bat}})^2}$$

Then  $\frac{dP}{dR_{\text{bat}}} = 0$  when  $R_{\text{bat}} = 0.2\Omega$ . From calculus, we know that this could be a maximum- you can check the sign of  $\frac{d^2P}{dR_{\text{bat}}^2}$  or plot  $P$  to convince yourself that it actually is a maximum.


Choosing  $R_{\text{bat}}$  to be 200m $\Omega$  will cause the resistance of the wire and  $R_{\text{bat}}$  in series to be 400m $\Omega$ , so by Ohm's law the current through the battery will be  $5/0.4 = 12.5\text{A}$ .

The battery has 8.36Wh, and the power dissipated across the battery is

$$P_{R_{\text{bat}}} = I_{R_{\text{bat}}}^2 \times R_{\text{bat}} = 12.5^2 \times 0.2 = 31.25\text{W}$$

so to get charging time we divide energy by power and get  $8.36/31.25 = 0.2675$  hours, or about 16 minutes. (Many thanks to Jia Cheng Lian for spotting the mistake in the original solutions.) Some batteries are designed to be charged quickly like this, but they must have carefully designed circuitry to prevent overheating- if charged too fast for too long, the battery could explode!

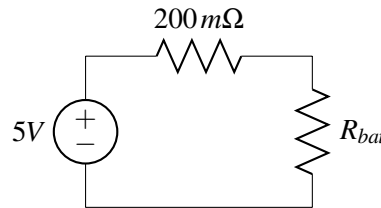Also note (by symmetry) that just as much power is dissipated across the wire as reaches the battery. Charging the battery quickly might be convenient, but it seems to waste a lot of energy.



Model of wall plug, wire, and battery.

- (g) (Bonus) You might have found that the answer for the previous section seemed to waste a lot of energy. If you don't forget to charge your phone overnight, you have all 8 hours that you spend sleeping to charge your phone. What should you choose for  $R_{\text{bat}}$  to minimize the amount of wasted energy, while still charging the battery in no longer than 8 hours? Compare the power dissipated across the wire and the power dissipated across  $R_{\text{bat}}$ . Use the same model from Fig. ??

**Solution:** Some of the power will be dissipated across the wire, and some will be dissipated across the battery. We want to maximize the fraction of power that reaches the battery. The power dissipated across the whole circuit is  $I_R^2(R_{\text{bat}} + 0.2)$  (where the second term is the equivalent resistance of the wire and battery in series). The power dissipated across the battery is  $I_R^2 R_{\text{bat}}$ . We want to maximize

$$\frac{I_R^2 R_{\text{bat}}}{I_R^2 (R_{\text{bat}} + 0.2)} = \frac{R_{\text{bat}}}{R_{\text{bat}} + 0.2} = \frac{1}{1 + 0.2/R_{\text{bat}}}$$

Clearly, this is an increasing function that approaches 1 as  $R_{\text{bat}}$  approaches  $\infty$ , so we want to make  $R_{\text{bat}}$  as large as possible. However, we cannot make  $R_{\text{bat}}$  too large, or the battery won't be charged in the 8 hour time limit. What is the largest  $R_{\text{bat}}$  that will still charge in 8 hours?

The battery is 2200mAh at 3.8V, so to charge in 8 hours we need to charge  $2.2 \times 3.8$  Wh of energy.

The power dissipated across the battery is  $I^2 R_{\text{bat}} = \left( \frac{5}{0.2 + R_{\text{bat}}} \right)^2 R_{\text{bat}}$ . Then we want

$$8 \text{ hours} = \frac{E}{P} = 2.2 \times 3.8 \times \frac{(0.2 + R_{\text{bat}})^2}{25 R_{\text{bat}}}$$

Solving, we get  $R_{\text{bat}} = 0.0017$  or  $23.52$ , and choose the larger value,  $23.52\Omega$ .

In the previous part, only half of the power reached the battery. By choosing a larger  $R_{\text{bat}}$ , a much bigger fraction of the power reaches the battery (although the total power is smaller). The fraction of power that reaches the battery is  $\frac{1}{1 + 0.2/23.52} \approx 0.99$ , almost 99%.

(Many thanks to Tony Situ, Daniel Ho, and Julian Chi-Kin Chan for catching the mistake in the original solutions.)

#### 4. Temperature Sensor

Measuring quantities in the physical world is the job of sensors. This means somehow extracting that information from the world and then converting it into a form that can be observed and processed. Electric circuits can be very useful for doing this.



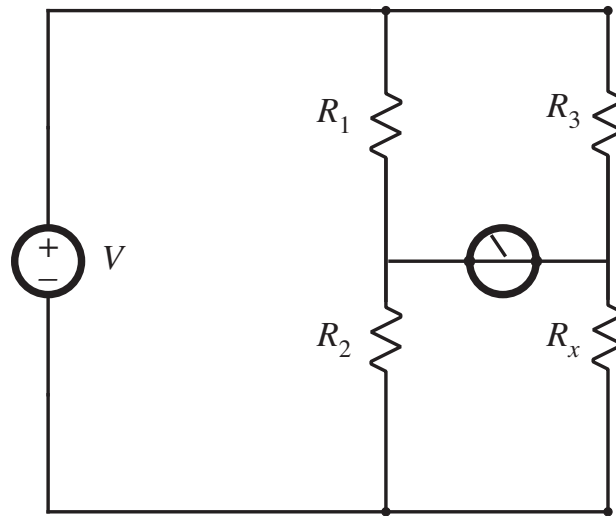


Figure 1: Circuit to measure resistance.

For most materials, resistance increases with increasing temperature; that is, a resistor has higher resistance when it is hot than when it is cold. This is often an annoyance to circuit designers who want their circuits to work the same way at different temperatures, but this fact can also be useful. It allows us to convert temperature, a “physical” quantity, into resistance, an “electrical” quantity, to build an electronic thermometer.

A PT100 is a special resistor made out of platinum that has a very precise relationship between resistance and temperature. At  $0^\circ\text{C}$ , the PT100 is a  $100\Omega$  resistor. Taking the data from <http://www.hayashidenko.co.jp/en/info12.html>, we found that the positive temperature coefficient for a PT100 is approximately  $0.366\Omega/^\circ\text{C}$ , that is, an increase in temperature of  $1^\circ\text{C}$  increases the PT100’s resistance by  $0.366\Omega$ .

Consider the circuit in Fig. 1. It allows measuring resistance very precisely, as we will see below. The circle in the middle of the resistors is a *galvanometer*. It functions like an ideal wire<sup>2</sup>, but it also detects any current going through it.

- (a) We say that the circuit is balanced when the current across the galvanometer in the middle is 0. Derive a relationship for the unknown resistance  $R_x$  in terms of the other three resistances if this is the case.

**Solution:** If there is no current across the galvanometer, then by KCL the current through  $R_1$  is equal to the current through  $R_2$  (call it  $i_{12}$ ) and the current through  $R_3$  is equal to the current through  $R_x$  (call it  $i_{3x}$ ). Because the galvanometer acts like an ideal wire, the voltage across  $R_2$  is the same as the voltage across  $R_x$ , so by Ohm’s law we know

$$i_{12}R_2 = i_{3x}R_x$$

Similarly, by KVL we know the voltage across  $R_1$  is the same as the voltage across  $R_3$ . Then by Ohm’s law we also know

$$i_{12}R_1 = i_{3x}R_3$$

<sup>2</sup> In fact, galvanometers can be constructed as essentially just a coil of wire – current passing through the coil creates a magnetic field, which deflects the needle of a compass according to the strength and direction of the current. This is another wonderful property of electricity – it can be harnessed to have physical macroscale-level effects on the world that are observable by people.

Then

$$\frac{i_{12}}{i_{3x}} = \frac{R_x}{R_2} = \frac{R_3}{R_1}$$

and

$$R_x = R_2 \frac{R_3}{R_1}$$

- (b) We can thus find one resistance if we know the other three. Suppose  $R_1 = 50\Omega$ ,  $R_3 = 100\Omega$  and  $R_2$  can be adjusted from 0 to  $300\Omega$ . This adjustment can be used to balance the circuit. What is the maximum resistance that can thus be measured for  $R_x$ ? (Only using the fact that the circuit is balanced when  $R_2$  is set appropriately).

**Solution:**  $\frac{R_3}{R_1} = 2$ , so to be balanced we need  $R_x = 2R_2$ . The largest  $R_x$  that can still be balanced by adjusting  $R_2$  is  $2 \times \max(R_2) = 2 \times 300 = 600\Omega$ .

- (c) Assume  $R_x$  in fig. 1 is a PT100. Give a procedure by which you can find the temperature of the resistor. What is the maximum temperature you can measure, and why?

**Solution:**  $R_x$  is a PT100, so if we measure  $R_x$  we can find temperature by  $T = \frac{R_x - 100}{0.366}$  ( $T$  in  $^{\circ}\text{C}$ ). We know  $R_x = 2R_2$  when current through the galvanometer is 0, so we have

$$T = \frac{2R_2 - 100}{0.366}$$

Then the procedure is to adjust  $R_2$  until the current across the galvanometer is 0, then look at what value  $R_2$  is, and compute  $T$  from  $R_2$ . Note that if positive current is flowing through the galvanometer from left to right, then  $R_2$  is too big, and if positive current is flowing through the galvanometer from right to left, then  $R_2$  is too small (the last section of this problem will discuss this more in depth). Because the max  $R_2$  is  $300\Omega$ , the maximum temperature that can be measured is

$$T = \frac{\max(R_x) - 100}{0.366} = \frac{2\max(R_2) - 100}{0.366} = 1366^{\circ}\text{C}$$

- (d) Suppose the company manufacturing your resistors gave you some parts from a bad batch, and instead of being  $100\Omega$ ,  $R_3$  was actually some random number between  $95$  and  $105\Omega$  (i.e.  $R_3 = (1 + \epsilon)100\Omega$  for  $|\epsilon| \leq 0.05$ ). Unfortunately, you didn't realize this and assumed it was still  $100\Omega$ . What is the biggest (in magnitude) error this will introduce to your temperature measurement?

**Solution:** The formula that will be used to measure temperature using the nominal value of  $R_3 = 100\Omega$  is

$$T_{\text{measured}} = \frac{2R_2 - 100}{0.366}$$

Using the true value of  $R_3$ , we have for zero current across the galvanometer that

$$R_x = R_2 \frac{(1 + \epsilon)100\Omega}{50\Omega} = 2(1 + \epsilon)R_2$$

Then the true temperature is measured as

$$T_{\text{true}} = \frac{2(1 + \epsilon)R_2 - 100}{0.366}$$

and the difference between the measured and the true is

$$T_{\text{true}} - T_{\text{measured}} = \frac{2\epsilon R_2}{0.366}$$

This error is biggest when  $R_2$  is biggest and  $|\varepsilon|$  is biggest, so the largest error is

$$2 \times (\pm 0.05) \times \frac{300\Omega}{0.366\Omega/^{\circ}C} = \pm 81.97^{\circ}C$$

- (e) Now assume both  $R_1$  and  $R_3$  came from the same bad batch, so

$$\begin{aligned} R_1 &= (1 + \varepsilon)50\Omega \\ R_3 &= (1 + \varepsilon)100\Omega \end{aligned}$$

where both  $R_1$  and  $R_3$  have the same  $\varepsilon$  (still  $|\varepsilon| \leq 0.05$ ). How much error will this introduce to the temperature measurement?

**Solution:** This will introduce no error to the temperature measurement! To see this, note that the condition for zero current across the galvanometer is

$$R_x = R_2 \frac{R_3}{R_1} = R_2 \frac{(1 + \varepsilon)100\Omega}{(1 + \varepsilon)50\Omega} = 2R_2$$

The  $1 + \varepsilon$ 's cancel out, so regardless of the size of the error, the relationship between  $R_x$  and  $R_2$  stays the same. If we repeat the previous part's  $T_{\text{true}} - T_{\text{measured}}$  calculation we find that the difference is always 0.

- (f) In the setup of the earlier parts (where  $R_1 = 50\Omega$  and  $R_3 = 100\Omega$  exactly), suppose we can only adjust  $R_2$  in increments of  $10\Omega$ . Assume the galvanometer displays the direction of current flow (or 0 if no current). By adjusting  $R_2$  in increments and observing the direction of current flow across the galvanometer, to what accuracy can we measure temperature?

**Solution:** We want to adjust  $R_2$  to balance  $R_x$  so there is no current across the galvanometer, but we can't choose  $R_2$  to be any value- it can only be moved in increments of  $10\Omega$ . Let's say  $R_2^*$  is the value of  $R_2$  that would balance the circuit- i.e.  $R_2^* = \frac{1}{2}R_x$ . Then  $R_2 = R_2^* + \Delta R_2$ , where  $\Delta R_2$  is an error term. If  $\Delta R_2 \neq 0$ , then the circuit will not be balanced and current will flow through the galvanometer.

Because the galvanometer acts like an ideal wire, the voltage across  $R_2$  is the same as the voltage across  $R_x$ , so by Ohm's law we know

$$i_2 R_2 = i_x R_x$$

Similarly, by KVL we know the voltage across  $R_1$  is the same as the voltage across  $R_3$ .

By KCL at the top junction between  $R_1$  and the voltage source, we know  $i_{\text{tot}} = i_1 + i_3$ , where  $i_{\text{tot}}$  is the total current out of the voltage source,  $i_1$  is the current through  $R_1$  and  $i_3$  the current through  $R_3$ . Then by Ohm's law we also know

$$i_1 R_1 = i_3 R_3$$

and conclude by substituting for  $i_3$  that

$$i_{\text{tot}} = i_1 \left( 1 + \frac{R_1}{R_3} \right)$$

Similarly,

$$i_2 R_2 = i_x R_x$$

and

$$i_{\text{tot}} = i_2 \left( 1 + \frac{R_2}{R_x} \right)$$

We chose  $R_2^*$  to balance the circuit according to the constraint  $R_2^* = R_x \frac{R_1}{R_3}$  so we can write

$$\begin{aligned} i_{tot} &= i_2 \left( 1 + \frac{R_2}{R_x} \right) \\ &= i_2 \left( 1 + \frac{R_2^* + \Delta R_2}{R_x} \right) \\ &= i_2 \left( 1 + \frac{R_1}{R_3} + \frac{\Delta R_2}{R_x} \right) \end{aligned}$$

Using the other equation for  $i_{tot}$ , we can find a relationship between  $\Delta R_2$  and the currents through  $R_1$  and  $R_2$ :

$$\begin{aligned} i_{tot} &= i_1 \left( 1 + \frac{R_1}{R_3} \right) \\ 1 + \frac{R_1}{R_3} + \frac{\Delta R_2}{R_x} &= \frac{i_1}{i_2} \left( 1 + \frac{R_1}{R_3} \right) \\ \Delta R_2 &= \left( \frac{i_1}{i_2} - 1 \right) \left( 1 + \frac{R_1}{R_3} \right) R_x \end{aligned}$$

Note that if the circuit is balanced,  $i_1 = i_2$  and we conclude that  $\Delta R_2 = 0$ , i.e. we have found the correct  $R_2$  such that  $R_2 = R_2^* = R_x \frac{R_1}{R_3}$ . Of course, since we can't exactly specify  $R_2$ , there will be some  $\Delta R_2 \neq 0$ . If  $i_1 < i_2$ , then some current going through  $R_3$  is crossing through the galvanometer and going through  $R_2$ , and  $\Delta R_2 < 0$ , so we want to increase the resistance of  $R_2$  to try to get closer to balance. Our galvanometer tells us the direction of the current, so if positive current goes from right to left, we conclude we need to increase  $R_2$ . If  $i_1 > i_2$ , then  $\Delta R_2 > 0$  and we have the opposite problem: we need to reduce  $R_2$  to get closer to balance.

Then by sweeping the all the values of  $R_2$ , we can find the values of  $R_{2,low}$  (where positive current flows through the galvanometer from right to left, but increasing  $R_2$  by  $10\Omega$  results in the current changing direction), and  $R_{2,high}$  (where positive current flows through the galvanometer from left to right, but decreasing  $R_2$  by  $10\Omega$  results in the current changing direction). We know that  $R_{2,low}$  and  $R_{2,high}$  are both within  $10\Omega$  of  $R_2^*$  and  $R_{2,low} + 10\Omega = R_{2,high}$ .

$$T_{true} = \frac{2R_2^* - 100}{0.366}$$

so

$$\frac{2R_{2,low} - 100}{0.366} \leq T_{true} \leq \frac{2R_{2,high} - 100}{0.366}$$

which we can write as

$$\frac{2(R_2^* + \Delta R - 10\Omega) - 100}{0.366} \leq T_{true} \leq \frac{2(R_2^* + \Delta R) - 100}{0.366}$$

with  $0 \leq \Delta R \leq 10\Omega$ . Subtracting  $T_{true}$  from each expression, we find that the error is in the interval

$$\left[ \frac{2(\Delta R - 10)}{0.366}, \frac{2\Delta R}{0.366} \right]$$

Because we don't know the magnitude of the current from the galvanometer, we can't tell which of the two estimates for  $T$  is closer. Our best guess is to pick the average of the two estimates. Averaging the two endpoints will have error


$$\frac{1}{2} \left( \frac{2(\Delta R - 10)}{0.366} + \frac{2\Delta R}{0.366} \right) = \frac{2(\Delta R - 5)}{0.366}$$

with  $0\Omega \leq \Delta R \leq 10\Omega$ , so the error of our temperature estimate will be

$$\pm \frac{10\Omega}{0.366 \frac{\Omega}{^\circ\text{C}}} = \pm 27.32^\circ\text{C}$$
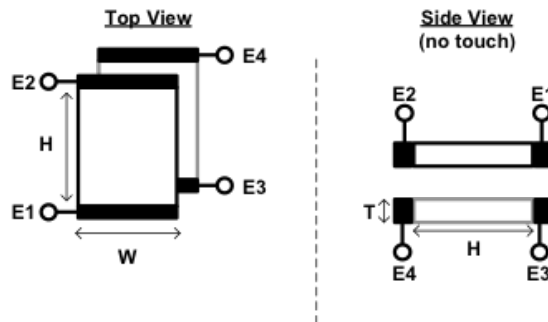
## 5. Multitouch Resistive Touchscreen

In this problem we will look at a simplified version of the multitouch resistive touchscreen. In particular, rather than measuring the position of two potential touch points in both dimensions (i.e., a pair of coordinates  $(x_1, y_1)$  and  $(x_2, y_2)$  corresponding to two touch positions), let's think about a version where we are interested in measuring only the vertical position of the two touch points (i.e.,  $y_1$  and  $y_2$ ). Therefore, unlike the touchscreens we looked at in class and as shown below, both of the resistive plates (i.e., both the top and the bottom plate) would have conductive strips placed along their top and bottom edges.




- (a) Assuming that both of the plates are made out of a material with  $\rho = 1\Omega m$  and that the dimensions of the plates are  $W = 3cm$ ,  $H = 12cm$ , and  $T = 0.5mm$ , with no touches at all, what is the resistance between terminals  $E_1$  and  $E_2$  (which would be the same as the resistance between terminals  $E_3$  and  $E_4$ )?


**Solution:**

$$\begin{aligned} R &= \rho \cdot \frac{L}{A} \Rightarrow R_{E_1-E_2} = \rho \left( \frac{H}{W \cdot T} \right) \\ R_{E_1-E_2} &= 1\Omega m \left( \frac{12 \times 10^{-2} m}{3 \times 10^{-2} \cdot 0.5 \times 10^{-3} m} \right) \\ R_{E_1-E_2} &= 8k\Omega \end{aligned}$$

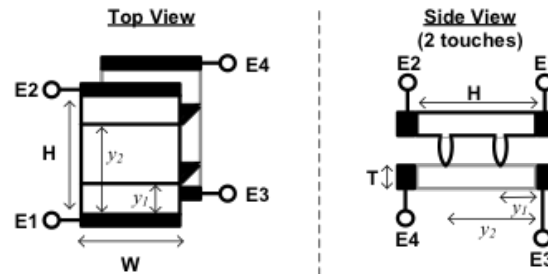- (b) Now let's look at what happens when we have two touch points. Let's assume that at wherever height the touch occurs, a perfect contact is made between the top plate and the bottom plate along the entire width of the plates (i.e., you don't have to worry about any lateral resistors), but that otherwise none of the electrical characteristics of the plates change. Defining the bottom of the plate as being  $y = 0\text{cm}$  (i.e., a touch right at  $E_1$  would be at  $y = 0\text{cm}$ ), let's assume that the two touches happen at  $y_1 = 3\text{cm}$  and  $y_2 = 7\text{cm}$ , and that your answer to part (a) was  $5\text{k}\Omega$  (which may or may not be the right answer), draw a model with 6 resistors that captures the electrical connections between  $E_1, E_2, E_3$ , and  $E_4$ . Note that for clarity, the system has been redrawn below to depict this scenario.



**Solution:**

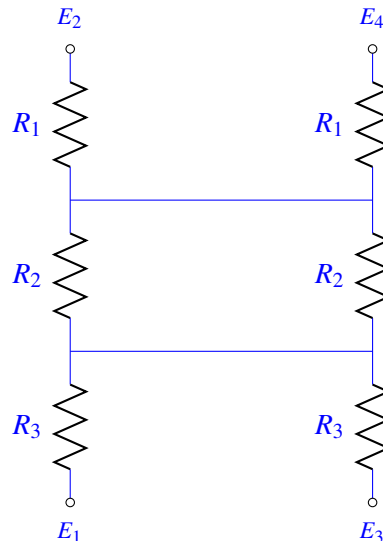


$$R_3 = \frac{3\text{cm}}{12\text{cm}} \cdot R_{E2-E1} = 1.25\text{k}\Omega$$

$$R_2 = \frac{7\text{cm} - 3\text{cm}}{12\text{cm}} \cdot R_{E2-E1} = 1.667\text{k}\Omega$$

$$R_1 = \frac{12\text{cm} - 7\text{cm}}{12\text{cm}} \cdot R_{E2-E1} = 2.0833\text{k}\Omega$$

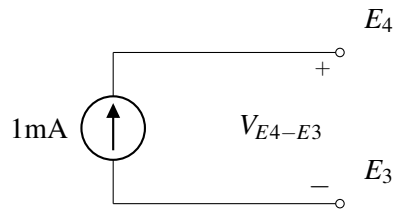- (c) Using the same assumptions as part b), if you drove terminals  $E_3$  and  $E_4$  with a  $1\text{mA}$  current source (as shown below) but left terminals  $E_1$  and  $E_2$  open-circuited, what is the voltage you would measure across  $E_4 - E_3$  (i.e.,  $V_{E4-E3}$ )?



**Solution:**


Equivalent resistance between  $E_4 - E_3$  is

$$\begin{aligned}
 R_{E4-E3} &= R_1 + R_2 \parallel R_2 + R_3 = R_1 + \frac{R_2}{2} + R_3 \\
 &= 1.25k\Omega + \frac{1.667k\Omega}{2} + 2.0833k\Omega \\
 &\approx 4.167k\Omega
 \end{aligned}$$

$$V_{E4-E3} = 1mA \cdot R_{E4-E3} \Rightarrow V_{E4-E3} = 4.167V$$

- (d) Now let's try to generalize the situation by assuming that the two touches can happen at any two arbitrary points  $y_1$  and  $y_2$ , but with  $y_1$  defined to always be less than  $y_2$  (i.e.,  $y_1$  is always the bottom touch point). Leaving the setup the same as in part c) except for the arbitrary  $y_1$  and  $y_2$ , by measuring only the voltage between  $E_4$  and  $E_3$ , what information can you extract about the two touch positions? Please be sure to provide an equation relating  $V_{E4-E3}$  to  $y_1$  and  $y_2$  as a part of your answer, and note that you may want to redraw the model from part (b) to help you with this.

**Solution:**

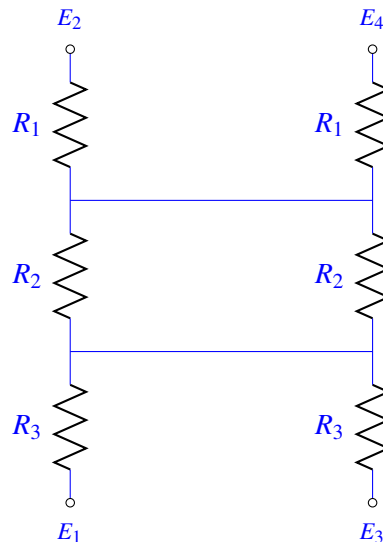

For general

$$\begin{aligned}
 R_3 &= \frac{y_1}{12cm} \cdot 5k\Omega \\
 R_2 &= \frac{y_2 - y_1}{12cm} \cdot 5k\Omega \\
 R_1 &= \frac{12cm - y_2}{12cm} \cdot 5k\Omega
 \end{aligned}$$

$$\begin{aligned}
 R_{E4-E3} &= R_1 + \frac{R_2}{2} + R_3 = \left( 12cm - y_2 + \frac{y_2 - y_1}{2} + y_1 \right) \cdot \frac{5k\Omega}{12cm} \\
 &= \left( 12cm + \frac{y_1}{2} - \frac{y_2}{2} \right) \cdot \frac{5k\Omega}{12cm}
 \end{aligned}$$

So


$$V_{E4-E3} = \frac{12cm - (y_2 - y_1)/2}{12cm} \cdot 5V$$

This means that by measuring  $V_{E4-E3}$ , we can only measure the distance between the two touch points  $(y_2 - y_1)$ .

- (e) One of your colleagues claims that by measuring the appropriate voltages, not only can they extract what both  $y_1$  and  $y_2$  are in this system, they can even do so in a way that would have a set of three independent voltage equations related to  $y_1$  and  $y_2$ . As we will see later, this will allow us to gain some robustness to noise in the voltage measurements.

In order to facilitate this, write equations relating  $V_{E4-E2}$  and  $V_{E1-E3}$  to  $y_1$  and  $y_2$ . (The third voltage we'll use is  $V_{E4-E3}$ , which you should have already derived an equation for in the previous part of the problem.)

**Solution:**

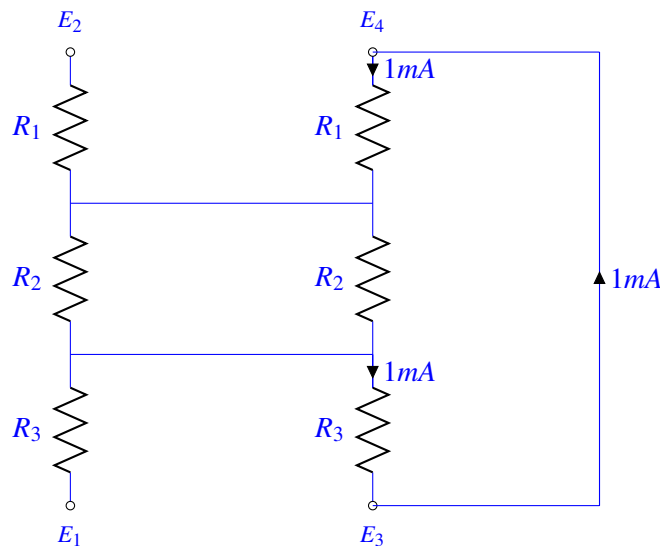

$$\begin{aligned}
 V_{E4-E2} &= I \cdot R_1 = \frac{12cm - y_2}{12cm} \cdot 5V \\
 V_{E1-E3} &= I \cdot R_3 = \frac{y_1}{12cm} \cdot 5V
 \end{aligned}$$

- 6. Your Own Problem** Write your own problem related to this week's material and solve it. You may still work in groups to brainstorm problems, but each student should submit a unique problem. What is the problem? How to formulate it? How to solve it? What is the solution?