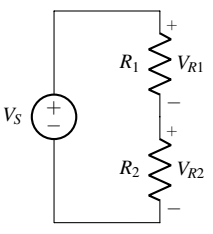
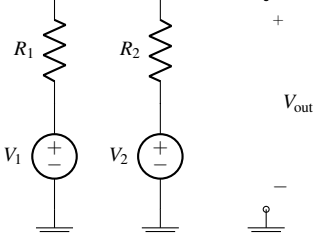
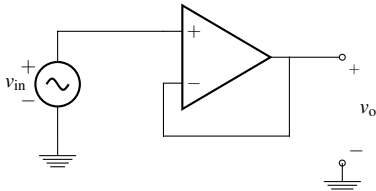
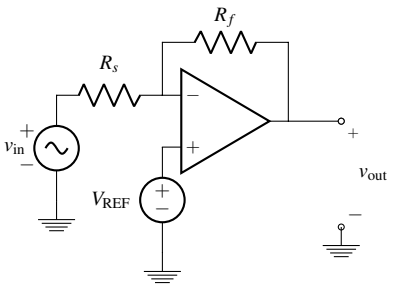
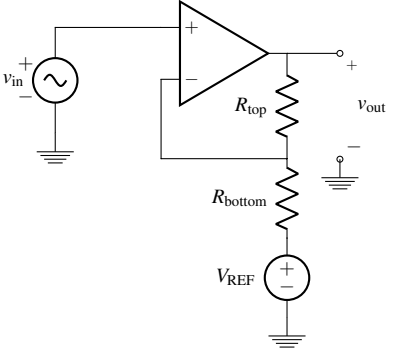
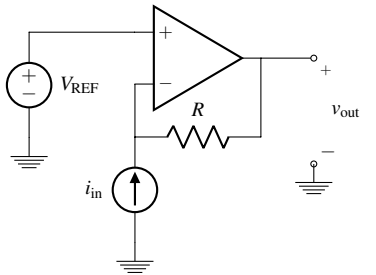


# EECS 16A Designing Information Devices and Systems I


## Spring 2020 Discussion 10A

### For Reference: Example Circuits

<p>Voltage Divider</p>  $V_{R2} = V_S \left( \frac{R_2}{R_1 + R_2} \right)$	<p>Voltage Summer</p>  $V_{out} = V_1 \left( \frac{R_2}{R_1 + R_2} \right) + V_2 \left( \frac{R_1}{R_1 + R_2} \right)$	<p>Unity Gain Buffer</p>  $\frac{v_{out}}{v_{in}} = 1$
<p>Inverting Amplifier</p>  $v_{out} = v_{in} \left( -\frac{R_f}{R_i} \right) + V_{REF} \left( \frac{R_f}{R_i} + 1 \right)$	<p>Non-inverting Amplifier</p>  $v_{out} = v_{in} \left( 1 + \frac{R_{top}}{R_{bottom}} \right) - V_{REF} \left( \frac{R_{top}}{R_{bottom}} \right)$	<p>Transresistance Amplifier</p>  $v_{out} = i_{in} (-R) + V_{REF}$

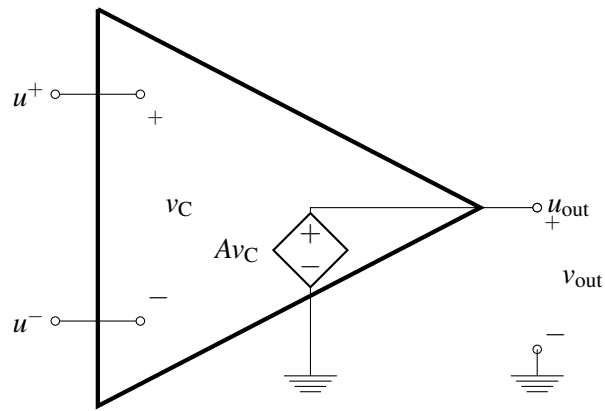
### 1. Op-Amp Rules and Negative Feedback Rule

Here is an equivalent circuit of an op-amp (where we are assuming that  $V_{SS} = -V_{DD}$ ) for reference:



- (a) What are the currents flowing into the positive and negative terminals of the op-amp (i.e., what are  $I^+$  and  $I^-$ )? Based on this answer, what are some of the advantages of using an op-amp in your circuit designs?
- (b) Suppose we add a resistor of value  $R_L$  between  $u_{out}$  and ground. What is the value of  $v_{out}$ ? Does your answer depend on  $R_L$ ? In other words, how does  $R_L$  affect  $Av_C$ ? What are the implications of this with respect to using op-amps in circuit design?

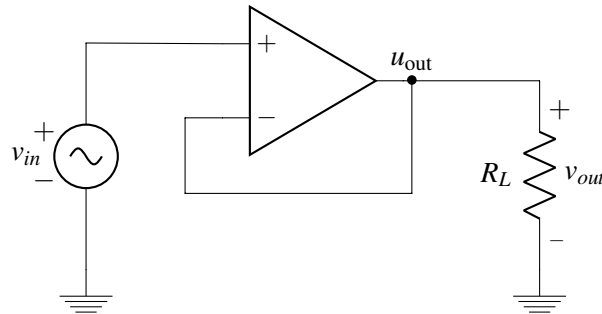
**For the rest of the problem, consider the following op-amp circuit in negative feedback:**



- (c) Assuming that this is an ideal op-amp, what is  $v_{out}$ ?
- (d) Draw the equivalent circuit for this op-amp and calculate  $v_{out}$  in terms of  $A$ ,  $v_{in}$ , and  $R_L$  for the circuit in negative feedback. Does  $v_{out}$  depend on  $R_L$ ? What is  $v_{out}$  in the limit as  $A \rightarrow \infty$ ?

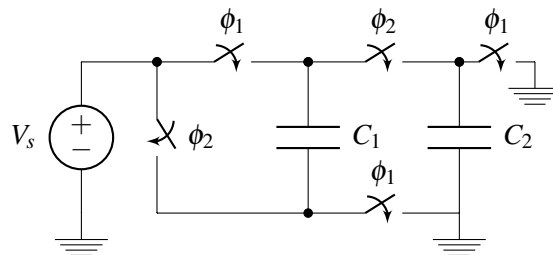
## 2. Charge Sharing Algorithm

For the switch capacitor circuit below, calculate the value of all node voltages at the end phase 2, as a function of the voltage source  $V_s$  and the capacitors  $C_1$ ,  $C_2$ .



### 3. Dividers for Days

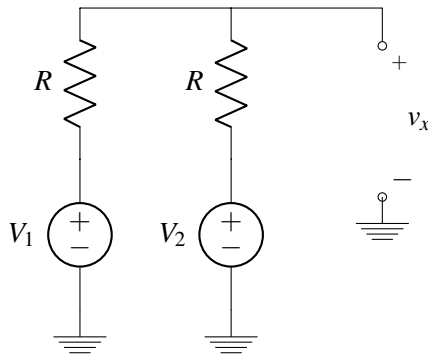(a) Solve the following circuit for  $v_x$ .



- (b) You have access to two voltage sources,  $V_1$  and  $V_2$ . You can use two resistors (as long as  $0 \leq R < \infty$ ). How would you design a circuit that produces a voltage  $v_x = \frac{1}{3}V_1 + \frac{2}{3}V_2$ ?
- (c) You have two current sources  $I_1$  and  $I_2$ . You also have a load resistor  $R_L = 6\text{ k}\Omega$ . Similar to the first part, you can use whatever resistors you want (as long as they are finite integer values). How would you design a circuit such that the current running through  $R_L$  is  $I_L = \frac{2}{5}(I_1 + I_2)$ ?