
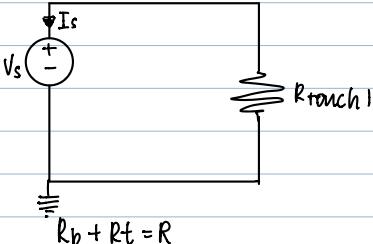


(a)

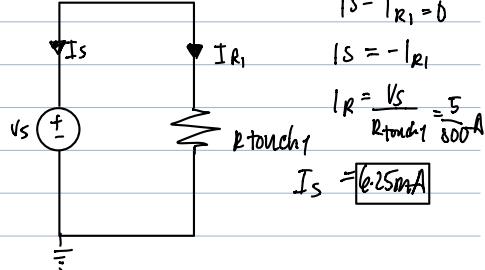

$$\begin{aligned} \text{b)} \quad R_{\text{touch}1} &= p_t \cdot \frac{l}{w \cdot t} \\ &= p_t \cdot \frac{l}{W \cdot t} \\ &= 0.5 \Omega \cdot \left(\frac{80 \times 10^{-3} \text{ m}}{90 \times 10^{-3} \text{ m} \cdot 1 \times 10^{-3} \text{ m}} \right) \\ &R_{\text{touch}1} = 800 \Omega \end{aligned}$$




$$I_S - I_{R_1} = 0$$

$$I_S = -I_{R_1}$$

$$I_R = \frac{V_S}{R_{\text{touch}1}} = \frac{5}{800} \text{ A}$$

$$I_S = 6.25 \text{ mA}$$

(c)

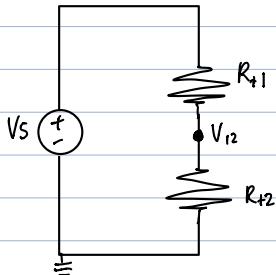

$$V_{12} = V_S \left(\frac{R_{t2}}{R_{t1} + R_{t2}} \right) = V_S \frac{y_2}{l} -$$

$$= 5 \cdot \frac{3}{4} \text{ V} \rightarrow 3.75 \text{ V}$$

$$R_{t1} = p_t \cdot \frac{l-y_2}{w_t} \quad R_{t2} = p_t \cdot \frac{y_2}{w_t}$$

$$\begin{aligned} \text{d)} \quad V_{ab} &= V_{x_1 y_1} - V_{x_2 y_2} \\ &= V_S \cdot \frac{R_{b1}}{R} - V_S \cdot \frac{R_{b2}}{R} \\ &= \frac{V_S}{R} (R_{b1} - R_{b2}) \\ &= V_S \left(\frac{R_{b1}}{R} - \frac{R_{b2}}{R} \right) \end{aligned}$$


$$\begin{aligned} \text{e)} \quad V_{ab} &= V_{x_1 y_1} - V_{x_2 y_1} \quad \text{since both the points are at the same vertical position} \\ &= V_S \left(\frac{R_{b1}}{R} - \frac{R_{b2}}{R} \right) \quad \frac{R_{b1}}{R} = \frac{R_{b2}}{R} = \frac{y_1}{L} \\ &\frac{R_{b1}}{R} - \frac{R_{b2}}{R} = 0 \end{aligned}$$

$$V_{ab} = 0$$

$$\begin{aligned} &= V_S \left(\frac{y_1}{L} - \frac{y_2}{L} \right) \\ &= 5 \left(\frac{30}{80} - \frac{10}{80} \right) \\ &= 5 \left(\frac{3}{8} \right) \\ &= \frac{-15}{8} \text{ V} = -1.875 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{f)} \quad V_{ab} &= V_{x_1 y_1} - V_{x_2 y_2} \\ &= V_S \left(\frac{R_{b1}}{R} - \frac{R_{b2}}{R} \right) \\ &= \frac{5}{80} (30 - 60) \\ &= -1.875 \text{ V} \\ &\text{absolute value } |V_{ab}| = 1.875 \text{ V} \end{aligned}$$

$$|V_{ab}| = \text{absolute value} = 1.875 \text{ V}$$

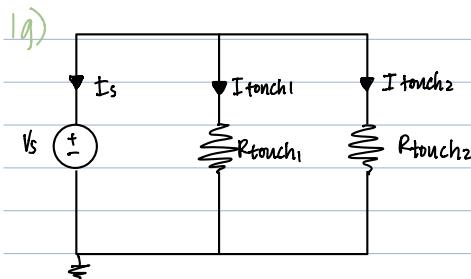


$$\begin{aligned} \text{h)} \quad I_S + I_{\text{touch}1} + I_{\text{touch}2} &= 0 \\ I_S &= -(I_{\text{touch}1} + I_{\text{touch}2}) \\ I_S &= \left(\frac{V_S}{R_{\text{touch}1}} + \frac{V_S}{R_{\text{touch}2}} \right) \end{aligned}$$

$$\begin{aligned} R_{\text{touch}2} &= \left(\frac{80 \times 10^{-3} \text{ m}}{70 \times 10^{-3} \text{ m} \cdot 1 \times 10^{-3} \text{ m}} \right) \\ R_{\text{touch}2} &= 457.142857 \Omega \end{aligned}$$

$$I_S \approx -(6.25 \text{ mA} + 10.94 \text{ mA}) = -17.19 \text{ mA}$$

$$\text{i)} \quad I_{\text{wire}} = \frac{V_{12 \text{ touch}1} - V_{22 \text{ touch}2}}{R_{\text{wire}}} = 0$$


2)

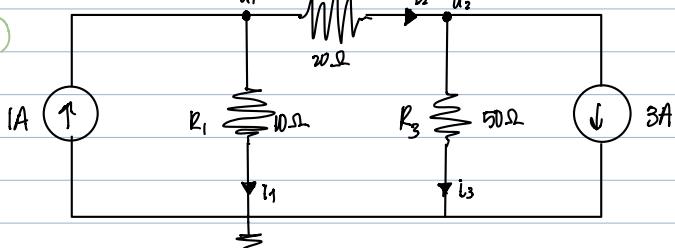

$$i_1 = \frac{-10 \text{ V}}{10 \Omega} = -1 \text{ A}$$

$$i_2 = \frac{-10 \text{ V} - (-50 \text{ V})}{20 \Omega} = 2 \text{ A}$$
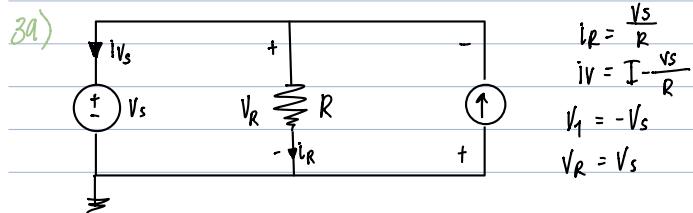
$$i_3 = \frac{-50 \text{ V}}{50 \Omega} = -1 \text{ A}$$



$$\begin{aligned} i_R &= \frac{V_S}{R} \\ i_V &= I - \frac{V_S}{R} \\ V_1 &= -V_S \\ V_R &= V_S \end{aligned}$$

$$\begin{aligned} P_{Vs} &= V_S i_V = \frac{1}{2} V_S^2 - \frac{V_S^2}{R} \\ R_1 &= I V_1 = -I V_S \\ P_R &= i_R V_R = \frac{V_S^2}{R} \end{aligned} \quad \left. \right\} = 0$$

$$3b) P_{VS} = (0.005A)(5V) - \frac{(5V)^2}{5000\Omega} = [0.02W]$$

$$P_I = -(0.005A)(5V) = [-0.025W]$$

$$P_R = \frac{5V^2}{5000\Omega} = [0.005W]$$

$$P_I = 40mW$$

$$P_{VS} = (-0.008A)(5V) - \frac{(5V)^2}{5000\Omega} = [-0.045W]$$

$$P_I = -(-0.008A)(5V) = [0.04W]$$

$$P_R = \frac{5V^2}{5000\Omega} = [0.005W]$$

$$P_{VS} + P_I + P_R = 0$$

4a) time required for the battery to discharge under typical usage conditions

$$\frac{\text{Battery rating}}{\text{current delivered}} = \frac{2770}{\left(\frac{0.5}{3.8}\right) \times 10^{-3}} = [35.04]$$

4b) charge stored in the battery when it is fully charged = ?

From the battery rating of 2770mAh

We have $I = 1,000mA = 1A$

$$t = 2.77 \text{ hrs} = 9972 \text{ sec}$$

We know $q = it$ (coulomb)

where q = charge stored

i = value of current

t = time

$$\therefore q = i \times t = 1 \times 9972 = [9972 \text{ coulomb}]$$

4c) When the battery is completely recharged the energy stored in the battery is given by

$$E = P \times t$$

$$\text{given } P = 3.8W$$

$$t = 2.77 \text{ hours}$$

$$\therefore E = 3.8 \times 2.77 = [10.526 \text{ W-h}]$$

$$\therefore E = 10.526 \times 3600 \text{ Joules}$$

$$\therefore E = [37893.6 \text{ Joules}]$$

4d) For 1 full charge

$$\text{energy consumption} = \frac{(Ah) \times V}{1000} \text{ unit}$$

$$= \frac{2.77 \times 3.8}{1000} = [0.010526 \text{ kWh}]$$

so for 31 days energy consumed

$$= 31 \times 0.010526 \text{ kWh}$$


$$= [0.326306 \text{ kWh}]$$

$$\text{cost of electricity} = 0.12 \text{ \$/kWh}$$

$$\text{cost of recharging} = 0.326306 \times 0.12$$

$$= [\$0.039]$$

4e)

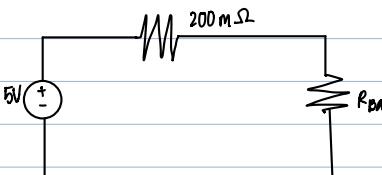

$$\text{For } R_{BAT} = 1 \text{ m}\Omega$$

$$I = \frac{5}{1.2} = 4.167 \text{ Amp}$$

to power dissipated across R_{BAT}

$$= I^2 R \\ = (4.167)^2 \times 1 \cdot 10^{-3} \text{ W}$$

$$\text{For } R_{BAT} = 1 \Omega$$

$$I = \frac{5}{201 \times 10^{-3}}$$

$$I = 24.87 \text{ A}$$

the power supplied to phone battery while

$$\text{charging} = I^2 R$$

$$= 17.3638 \text{ W}$$

time taken by battery to charge = $\frac{2.77}{4.87} \text{ hours}$

$$= 0.66 \text{ hours}$$

$$= (24.87)^2 \times (1 \times 10^{-3}) \text{ W}$$

$$= 0.618 \text{ W}$$

time taken by battery to charge

$$= \frac{\text{Battery A-h}}{\text{charging current}}$$

$$\frac{2.77}{24.87} \text{ h} = 0.11 \text{ hours}$$

for $R_{bat} = 10 \text{ k}\Omega$

$$I = \frac{5}{10,000 \cdot 2} = 4.99 \times 10^{-4} \text{ A}$$

$$I = 0.499 \text{ mA}$$

so the power is dissipated across R_{bat}

$$= I^2 R$$



$$(4.99 \times 10^{-4})^2 \times 10,000$$

$$= 2.499 \times 10^{-3} \text{ W}$$

time taken by the battery to charge

$$= \frac{2.77}{4.99 \times 10^{-4}}$$



$$= 5551.10 \text{ hours}$$

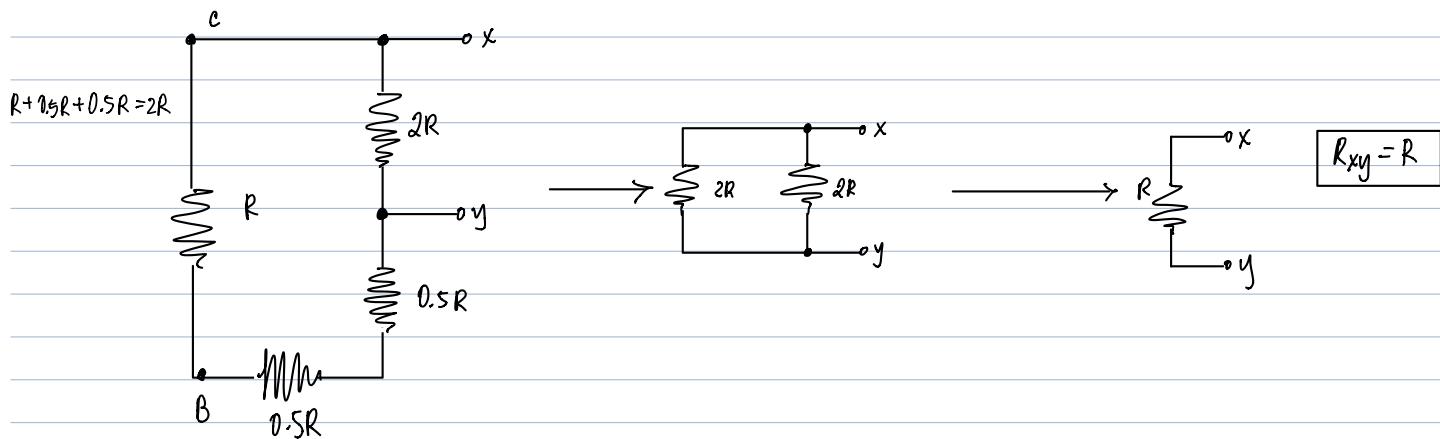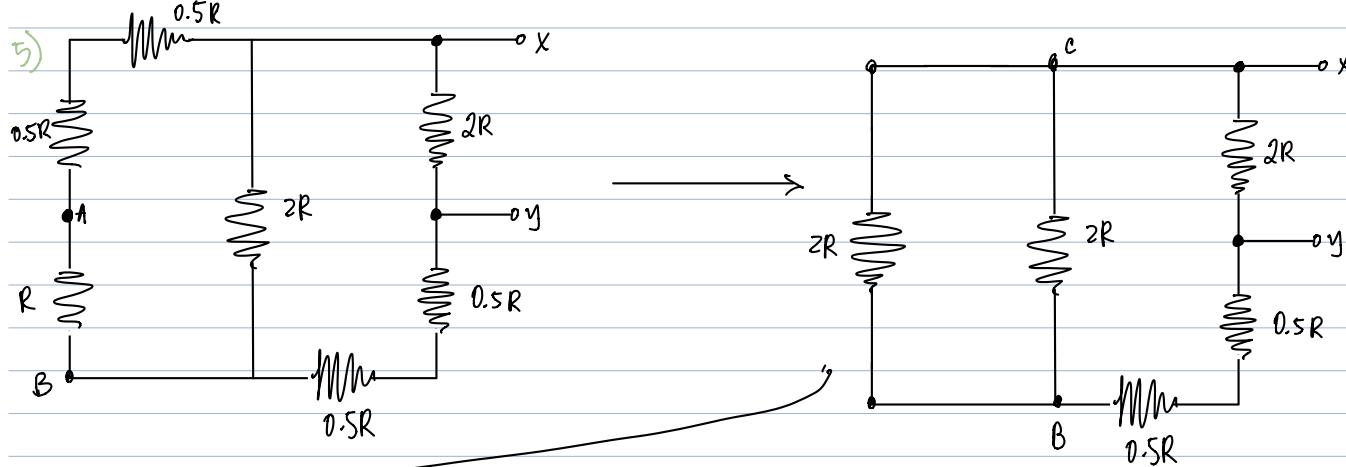

$$(e) i = \frac{1}{3}A$$

① turn off 1A current source

② turn off 5V voltage source

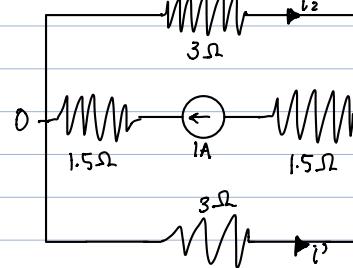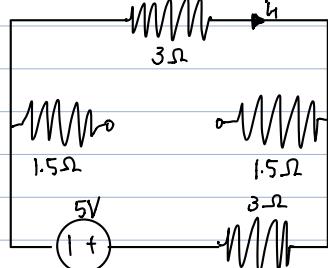

$$1 - i_2 - i^3 = 0$$

$$i_2 = \frac{1}{2}A$$

$$i = i_1 + i_2 = -\frac{5}{6}A + \frac{1}{2}A = -\frac{1}{3}A$$

7) the I_s current flowing through C_1 is also the same flowing through C_2 . $V_{out}(0)=0$

$$\begin{aligned} I_s = C_2 \frac{dV_{out}(t)}{dt} &= V_{out}(t) = \int \frac{I_s}{C_2} dt \\ &= \frac{I_s t}{C_2} + V_{out}(0) \\ &= \frac{I_s t}{C_2} \end{aligned}$$

8) I worked with Sadia Durashit (3004541667), 6 hours